

Roll No.	Simulation Assignment
1	Full Adder and Full Subtractor
2	Full Adder and Full Subtractor
3	Full Adder and Full Subtractor
4	Full Adder and Full Subtractor
5	2-Bit Comparator
6	2-Bit Comparator
7	2-Bit Comparator
8	2-Bit Comparator
9	Parity Even and Odd Circuit
10	Parity Even and Odd Circuit
11	Parity Even and Odd Circuit
12	Parity Even and Odd Circuit
13	D and J-K flip Flop
14	D and J-K flip Flop
15	D and J-K flip Flop
16	D and J-K flip Flop
17	T and D Flip Flop
18	T and D Flip Flop
19	T and D Flip Flop
20	T and D Flip Flop
21	8:1 MUX
22	8:1 MUX
23	8:1 MUX
24	8:1 MUX
25	3:8 Decoder
26	3:8 Decoder
27	3:8 Decoder
28	3:8 Decoder
29	Boolean Laws
30	Boolean Laws
31	Boolean Laws
32	Boolean Laws
33	Implementation of AND,OR and NOT using NAND Gates
34	Implementation of AND,OR and NOT using NAND Gates
35	Implementation of AND,OR and NOT using NAND Gates
36	Implementation of AND,OR and NOT using NAND Gates
37	8:3 Encoder
38	8:3 Encoder
39	8:3 Encoder
40	8:3 Encoder
41	Implenetation of Full Adder SUM and Carry boolean Expression using 4:1 MUX
42	Implenetation of Full Adder SUM and Carry boolean Expression using 4:1 MUX
43	Implenetation of Full Adder SUM and Carry boolean Expression using 4:1 MUX

44	Implenetation of Full Adder SUM and Carry boolean Expression using 4:1 MUX
45	Implenetation of Full Adder SUM and Carry boolean Expression using Decoder
46	Implenetation of Full Adder SUM and Carry boolean Expression using Decoder
47	Implenetation of Full Adder SUM and Carry boolean Expression using Decoder
48	Implenetation of Full Adder SUM and Carry boolean Expression using Decoder
49	S-R and J-K Flip Flop
50	S-R and J-K Flip Flop
51	S-R and J-K Flip Flop
52	S-R and J-K Flip Flop
53	1:8 DMUX
54	1:8 DMUX
55	1:8 DMUX
56	1:8 DMUX
57	Implementation of Even parity boolean expression using 4:1 MUX
58	Implementation of Even parity boolean expression using 4:1 MUX
59	Implementation of Even parity boolean expression using 4:1 MUX
60	Implementation of Even parity boolean expression using 4:1 MUX
61	Implementation of Odd parity boolean expression using decoder
62	Implementation of Odd parity boolean expression using decoder
63	Implementation of Odd parity boolean expression using decoder
64	Implementation of Odd parity boolean expression using decoder
65	Implenetation of Subtractor Difference and Borrow boolean Expression using Decoder
66	Implenetation of Subtractor Difference and Borrow boolean Expression using Decoder
67	Implenetation of Subtractor Difference and Borrow boolean Expression using Decoder
68	Implenetation of Subtractor Difference and Borrow boolean Expression using Decoder
69	Implenetation of Full Subtractor Difference and Borrow boolean Expression using 4:1 MUX
70	Implenetation of Full Subtractor Difference and Borrow boolean Expression using 4:1 MUX
71	Implenetation of Full Subtractor Difference and Borrow boolean Expression using 4:1 MUX
72	Implenetation of Full Subtractor Difference and Borrow boolean Expression using 4:1 MUX
73	Implementation of AND,OR and NOT using NOR Gates
74	Implementation of AND,OR and NOT using NOR Gates
75	Implementation of AND,OR and NOT using NOR Gates
76	Implementation of AND,OR and NOT using NOR Gates
77	Implementation of AND,OR and NOT using NOR Gates

